

Table 1: Circuit (a) Components (Series)

Power Supply: 125V DC
R1: Resistor, 20 Ohms
R2: Resistor, 30 Ohms
R3: Resistor, 50 Ohms

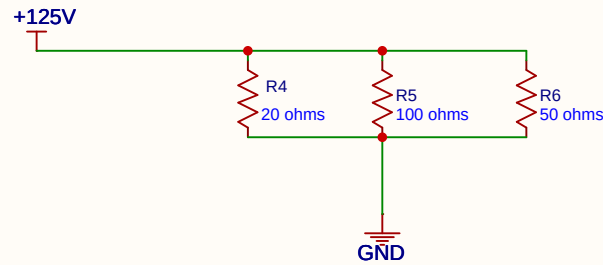


Table 2: Circuit (b) Components (Parallel)

Power Supply: 125V DC
R4: Resistor, 20 Ohms
R5: Resistor, 100 Ohms
R6: Resistor, 50 Ohms

TITLE: SCH_iot-assignment-basile_2026-10-05		REV: 1.0
EasyEDA	Company: Embedded Systems & IoT	Sheet: 1/1
	Date: 2026-10-04	Drawn By: makutano.basile